



Instructions

- You are allowed to use only those models that have been provided. You can download by clicking the name.
- Read the questions thoroughly.
- You can use previous lab reports and netlist.

Part-1

1. We want to build a good analog switch i.e. $V_{out} = V_{in}$, on resistance (R_{ON}) = $|V_{DS}/I_{DS}| = 0 \Omega$ for all V_{in} when control input is enabled. Consider $V_{DD} = 3.3 \text{ V}$
 - Write ngspice netlist for below PMOS pass gate having $W/L = 4 \mu\text{m}/0.4 \mu\text{m}$. Plot and comment on V_{out} vs V_{in} , R_{ON} vs V_{in} .
 - Similarly, write ngspice netlist for below NMOS pass gate having $W/L = 4 \mu\text{m}/0.4 \mu\text{m}$. Plot and comment on V_{out} vs V_{in} , R_{ON} vs V_{in} . Which MOSFET has higher R_{ON} and explain the reason?

 


Figure 1: PMOS transistor switch

 


Figure 2: NMOS transistor switch

- Write ngspice netlist for below transmission gate circuit with each MOSFET having $W/L = 4 \mu\text{m}/0.4 \mu\text{m}$, plot V_{out} vs V_{in} , R_{ON} vs V_{in} . Explain the reason for small peak in R_{ON} plot and mention the maximum value of R_{ON} . Change device parameters such that on-resistance on either side of the small peak is the same. Show both the plots of R_{ON} vs V_{in} before and after changing device parameters.
Note: Ignore the peak value of R_{ON} at V_{in} near 0 V for PMOS, NMOS, transmission gate plots

(1 +1 + 3 Marks)

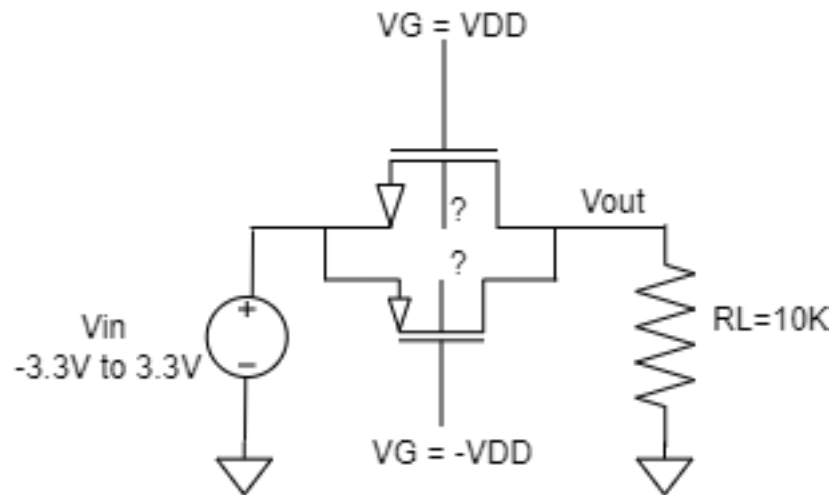


Figure 3: Transmission Gate Circuit

Note:For both part -1&2 questions use [PMOS_NMOS](#) model file, the same as you have used for CMOS inverter experiment in last lab (Click on the name)