

EE236: Experiment No. 5

PMOS I/V Characteristics and Applications

Mayur Ware, 19D070070

March 9, 2022

1 Overview of the experiment

1.1 Aim of the experiment

Aim of this experiment is to analyze the I-V characteristics of PMOS in linear region and saturation region by varying V_{GS} and V_{DS} .

To find the parameters of PMOS such as Threshold Voltage (V_T), Transconductance (g_m) and Body Effect Coefficient (γ).

1.2 Methods

Firstly, I read and understood the background material to understand the working and functionality of PMOS. Then, I wrote the ngspice netlist to plot the I_D vs V_{DS} characteristics of PMOS by varying V_{GS} from -2.5V to -4V in steps of -0.5V and V_{DS} from 0 V to -5 V

After that, I modified the netlist to plot I_D vs V_{GS} characteristics of PMOS in linear and saturation region to find Threshold Voltage (V_T), Transconductance (g_m). Finally, I modified the netlist again to analyze the Body Bias Effect on PMOS and calculated the Body Effect Coefficient (γ) by varying V_{SB} .

2 Design

I-V Characteristics of PMOS

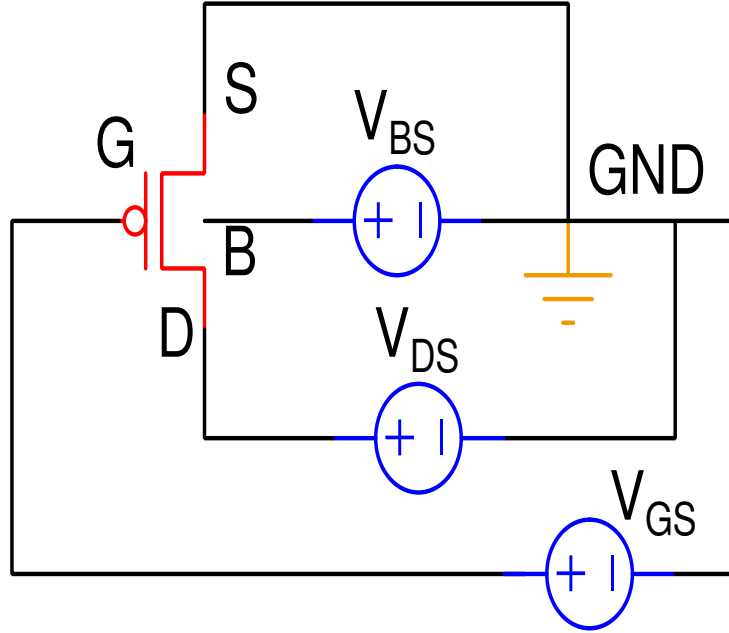


Fig 1. : I-V Characteristics of PMOS

The circuit in Fig. 1 is for the I-V characteristics simulation of PMOS. I did DC analysis for V_{DS} varied from -5V to 0V. Also, I varied V_{GS} from -2.5V to -4V in steps of -0.5V.

Then, I calculated R_{DS} in the linear region by plotting the graph and took the rightmost value to get most accurate R_{DS} (in linear region).

$$R_{DS} = \frac{V_{DS}}{I_{DS}} \quad (1)$$

Then, I calculated the early voltage (V_A) using the x-intercept of straight line on the saturation region. And using it, I calculated R_O .

$$V_A = \frac{1}{\lambda} \quad (2)$$

$$R_O = \frac{1}{\lambda I_{D(sat)}} \quad (3)$$

After that, in the I_D vs V_{GS} characteristics in linear region and saturation region, I found Threshold Voltage (V_T) using the point of intersection of the straight line with the x-axis. And I calculated Transconductance (g_m) using the slope of the straight line.

$$g_m = \frac{\delta I_D}{\delta V_{GS}} \quad (4)$$

Finally, I plotted I_D vs V_{GS} characteristics of PMOS by varying values of V_{SB} as 0V, -1V, -2V, -3V and -4V. Then, I calculated the value of Threshold Voltage (V_T) in all cases to plot V_T vs V_{SB} graph to find the value of Body Effect Coefficient (γ) using the given equation.

$$V_T = V_{T0} + \gamma(\sqrt{\Phi_s + V_{BS}} - \sqrt{\Phi_s}) \quad (5)$$

3 Simulation results

3.1 Code snippets

3.1.1 I_D - V_{DS} Characteristics of PMOS :

```
Mayur Ware | 19D070070
*EE236 | Lab 5 | Part 1
*I-V Characteristics of PMOS
.include pmos.txt ;Including PMOS model file
*Netlist
M1 D G GND GND ALD1107 ;Defining the PMOS Model Drain, Gate, Source,
Body
Vd D GND dc 0
*Vg G GND dc -4
*Vg G GND dc -3.5
*Vg G GND dc -3
Vg G GND dc -2.5
*DC Analysis
.dc Vd -5 0 0.1
.control
run
set color0 = white
set color1 = black
```

```

*set color2 = red
*set color2 = blue
*set color2 = yellow
set color2 = green
set xbrushwidth = 2
plot I(Vd) vs V(D) ;Id vs Vds plot
plot abs((V(D))/(I(Vd))) ;R_DS plot
.endc
.end

```

3.1.2 I_D - V_{GS} Characteristics of PMOS :

Mayur Ware | 19D070070

*EE236 | Lab 5 | Part 2

*Id-Vgs Characteristics of PMOS

.include pmos.txt ;Including PMOS model file

*Netlist

M1 D G GND GND ALD1107 ;Defining the PMOS Model Drain, Gate, Source,
Body

*Vd D GND dc -200m

Vd D GND dc -5

Vg G GND dc 0

*DC Analysis

.dc Vg -5 0 0.01

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red

set xbrushwidth = 2

plot I(Vd) vs V(G) ;Id vs Vgs plot

plot sqrt(I(Vd)) vs V(G) ;sqrt(Id) vs Vgs plot

.endc

.end

3.1.3 Effect of Body Bias :

Mayur Ware | 19D070070

*EE236 | Lab 5 | Part 3

*Id-Vgs Characteristics of PMOS

.include pmos.txt ;Including PMOS model file

```

*Netlist
M1 D G GND B ALD1107 ;Defining the PMOS Model Drain, Gate, Source,
Body
Vd D GND dc -200m
Vg G GND dc 0
*Vb B GND dc 0
*Vb B GND dc 1
*Vb B GND dc 2
*Vb B GND dc 3
Vb B GND dc 4
*DC Analysis
.dc Vg -5 0 0.01
.control
run
set color0 = white
set color1 = black
*set color2 = red
*set color2 = blue
*set color2 = yellow
*set color2 = green
set color2 = violet
set xbrushwidth = 2
plot I(Vd) vs V(G) ;Id vs Vgs plot
.endc
.end

```

3.2 Simulation results

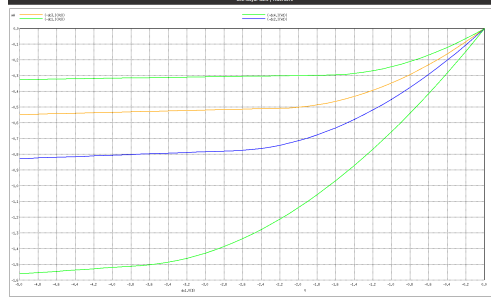


Fig. 2 : I_d - V_{ds} Characteristics of PMOS

For lower values of V_{DS} , PMOS is in the saturation mode. Whereas, after a certain value, PMOS is going into the linear region. Red, Blue, Yellow and Green curves are for V_{DS} values -4V, -3.5V, -3V and -2.5V respectively.

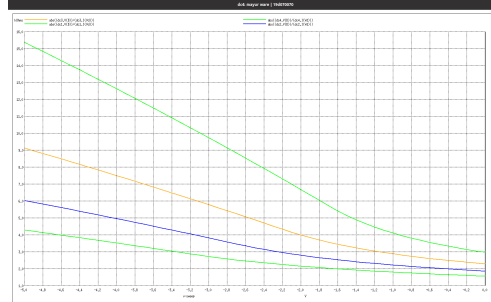


Fig. 3 : R_{DS} of PMOS

For lower values of V_{DS} , R_{DS} is decreasing linearly and then it is saturating at a value. The leftmost point of this graph would be the best value of R_{DS} . Red, Blue, Yellow and Green curves are for V_{DS} values -4V, -3.5V, -3V and -2.5V respectively.

V_{GS} (in V)	R_{GS} (in $k\Omega$)	$I_{D(sat)}$	R_O (in $k\Omega$)
-4	1.551	1.55mA	20.8
-3.5	1.844	0.82mA	39.0
-3	2.293	0.55mA	58.7
-2.5	2.965	0.32mA	87.8

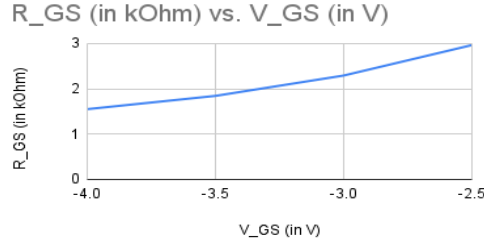


Fig. 4 : R_{GS} vs V_{GS}

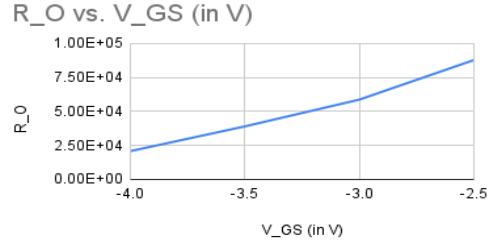


Fig. 5 : R_O vs V_{GS}

It can be seen in Fig. 4 and Fig. 5 that both R_{GS} and R_O increase with increase in V_{GS} .

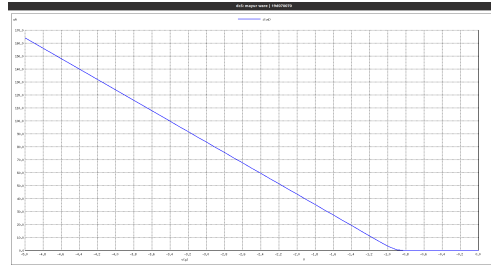


Fig. 6 : I_D vs V_{GS} Characteristics in linear mode of PMOS

Graph is a straight line with negative slope and I_D is decreasing with increase in V_{GS} .

Threshold Voltage (V_T) = -0.82V and Transconductance (g_m) = 4.2E-05.

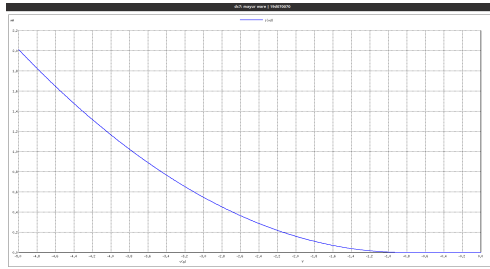


Fig. 7 : I_D vs V_{GS}

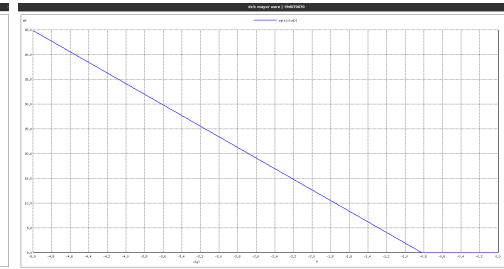


Fig. 8 : $\sqrt{I_D}$ vs V_{GS}

Saturation mode of PMOS

I_D vs V_{GS} curve is parabolic. Whereas, $\sqrt{I_D}$ vs V_{GS} curve is a straight line with negative slope. Both decrease with increase in V_{GS} .

Threshold Voltage (V_T) = -0.82V and Transconductance (g_m) = 6.96E-05 and $K = 0.228 \text{ mV/A}^2$

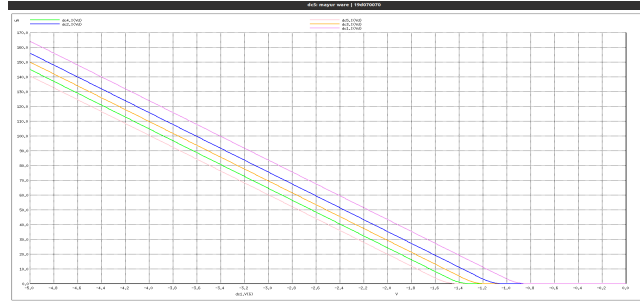


Fig. 9 : I_D vs V_{GS} Characteristics of PMOS varying V_{SB}

I_D vs V_{GS} Characteristics of PMOS varying V_{SB} are straight lines with negative slopes. Curves shift to left with decrease in V_{SB} .

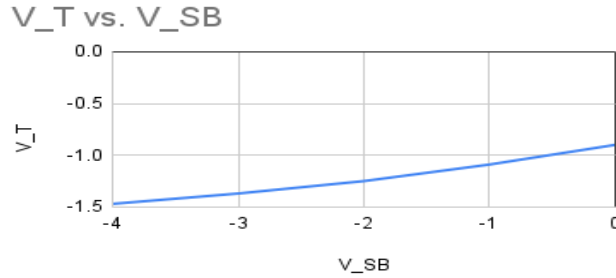


Fig. 10 : V_T vs V_{SB}

V_T increases with increase in V_{SB} . Using this graph and given equation, the value of Body Effect Coefficient (γ) comes out to be -0.465.

4 Experimental results

This section is not applicable for this experiment.

5 Experiment completion status

I have completed all sections as well as exercises in this lab.

6 Questions for reflection

This section is not applicable for this experiment.