

# EE236: Experiment No. 8

## Bipolar Junction Transistor

Mayur Ware, 19D070070

April 14, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

Aim of this experiment is to measure the forward active, reverse active parameters and DC output characteristics in common base (CB) and common emitter (CE) configurations. To plot the combined  $I_C$  and  $I_B$  vs  $V_{BE}$  of a BJT on a semi-log scale (Gummel plot) and  $\beta_{DC}$  v/s  $I_C$  characteristics for constant  $V_{BC}$ .

To calculate pi model small signal parameters ( $r_\pi$ ,  $g_m$  and  $r_o$ ) and analyse performance of BJT inverter at different frequencies.

### 1.2 Methods

Firstly, I wrote the netlist for BJT in CE configuration to plot  $I_C$  vs  $V_{CE}$  by varying  $I_B$  to calculate the parameters. Similarly, I did it for CB configuration to plot  $I_C$  vs  $V_{CB}$  by varying  $I_E$  to calculate the parameters. Then, I plotted the Gummel plot.

Then, I wrote the netlist of small signal model of BJT in CE configuration to calculate the small signal parameters using biasing the configuration. Finally, I simulated the switching behaviour of BJT at different frequencies in two different configurations.

## 2 Design

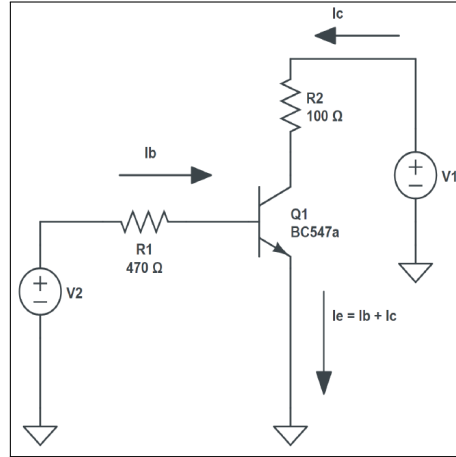


Fig. 1 : BJT in CE configuration

The circuit shown in Fig. 1 is used to plot the  $I_C$  vs  $V_{CE}$  characteristics of CE configuration. I determined the parameters  $\alpha$ ,  $\beta$ , Reverse  $\beta$  (RB) and Early Voltage ( $V_A$ ) by assuming  $\gamma = 1$ .  $I_B$  was varied from 0A to 1mA in steps of 0.1mA.

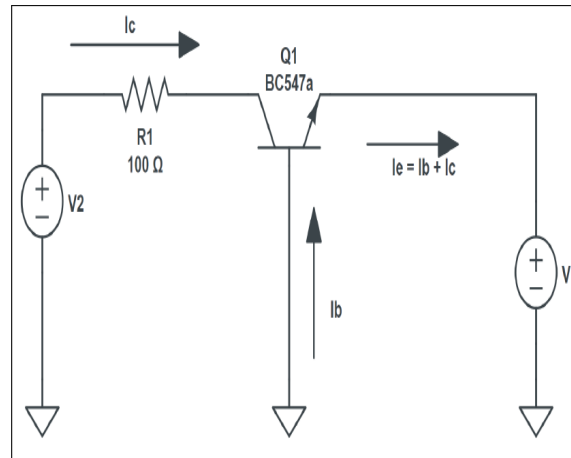


Fig. 2 : BJT in CB configuration

Fig. 2 shows the circuit used for characteristics of CB configuration similar to the previous circuit.  $I_E$  was varied from 0A to 10mA in steps of 1mA. Following are the equations used for both

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

Reverse  $\beta$  (RB) can be found by interchanging the terminals.

$$V_A = \frac{I_1 V_2 - I_2 V_1}{I_1 - I_2}$$

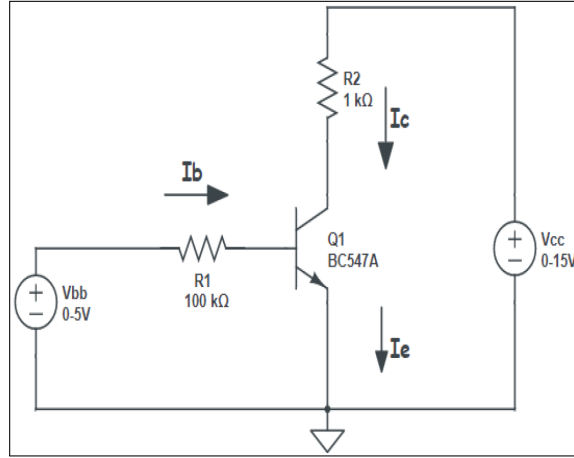



Fig. 3 : BJT Small Signal Parameters

The circuit shown in Fig. 3 is used to find the small signal parameters of BJT.  $V_{CC}$  was set to 9.5V and  $V_{BB}$  was chosen as 2.985V.

$$g_m = \frac{I_C}{V_t}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_C}$$

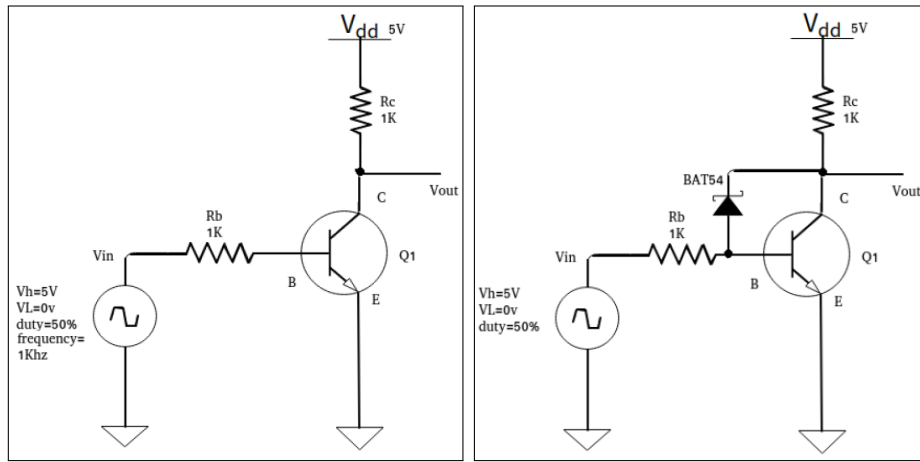

BJT switching circuit

Fig. 4 : without schottky diode      Fig. 5 : with schottky diode

Fig. 4 and Fig. 5 show the switching behaviour of BJT with and without schottky diode. Input was a pulse of 5V amplitude and 1kHz frequency which was later changed to 100kHz and 1MHz. The plots were obtained and turnoff time was found. Turnoff time is the sum of storage time, the delay between input zero and output at 90% max value, and rise time, the delay between 10% max output to 90% max output.

## 3 Simulation results

### 3.1 Code snippets

#### 3.1.1 BJT in CE configuration :

Mayur Ware | 19D070070

\*EE236 | Lab 8

\*BJT in CE Configuration

.include BC547.txt ;Including BJT model file

\*Netlist

Q1 C B E bc547a ;Defining the BJT Model Collector, Base, Emitter

R1 1 B1 470

R2 2 C1 100

V1 2 GND dc 0

V2 1 GND dc 0

Vc C1 C dc 0

```

Vb B1 B dc 0
Ve E GND dc 0
*DC Analysis
.dc V1 0 10 0.1 V2 0.7 1.17 0.047
.control
run
set color0 = white
set color1 = black
set color2 = blue
set xbrushwidth = 2
let V = V(C) - V(E)
plot I(Vc) vs V
plot I(Vc)/I(Ve) ;Base Transport Factor
plot I(Vc)/I(Vb) ;Beta
plot I(Ve)/I(Vb) ;Reverse Beta
.endc
.end

```

### 3.1.2 BJT in CB configuration :

Mayur Ware | 19D070070

\*EE236 | Lab 8

\*BJT in CB Configuration

.include BC547.txt ;Including BJT model file

\*Netlist

Q1 C B E bc547a ;Defining the BJT Model Collector, Base, Emitter

R1 1 C1 100

Ie E E1 dc 1m

V1 E1 GND dc 0

V2 1 GND dc 0

Vc C1 C dc 0

Vb B GND dc 0

\*DC Analysis

.dc V2 -2 10 0.1 Ie 0m 10m 1m

.control

run

set color0 = white

set color1 = black

set color2 = blue

```

set xbrushwidth = 2
let V = V(C) - V(B)
plot I(Vc) vs V
plot I(Vc)/I(V1) ;Base Transport Factor
plot I(Vc)/I(Vb) ;Beta
plot I(V1)/I(Vb) ;Reverse Beta
.endc
.end

```

### 3.1.3 Gummel Plot :

Mayur Ware | 19D070070

\*EE236 | Lab 8

\*Gummel Plot

.include BC547.txt ;Including BJT model file

\*Netlist

Q1 C B GND bc547a ;Defining the BJT Model Collector, Base, Emitter

Vin In 0 5

V1 1 In 5

Rc 2 1 100

Rb 3 In 470

Vc 2 C 0

Vb 3 B 0

\*DC Analysis

.dc Vin 0.2 1.2 10m

.control

run

set color0 = white

set color1 = black

set color2 = blue

set xbrushwidth = 2

plot log(i(Vc)) vs V(3) log(abs(i(Vb))) vs V(3)

let beta = log(i(Vc)) - log(abs(i(Vb)))

plot beta vs i(Vc)

.endc

.end

### 3.1.4 BJT switching behaviour without schottky diode :

Mayur Ware | 19D070070

```

*EE236 | Lab 8
*Switching Behavior
.include BC547.txt ;Including BJT model file
.include 2N3904.txt
*Netlist
*Q1 C B GND bc547a ;Defining the BJT Model Collector, Base, Emitter
Q1 C B GND 2n3904c
Vin In 0 PULSE(0 5 0 0 0 5u 10u)
Rb In B 1k
Rc 2 C 1k
V_dd 2 0 5
*Transient Analysis
.tran 1u 5u
.control
run
set color0 = white
set color1 = black
set color2 = blue
set xbrushwidth = 2
plot V(C) V(In)
.endc
.end

```

### 3.1.5 BJT switching behaviour with schottky diode :

Mayur Ware | 19D070070

```

*EE236 | Lab 8
*Switching Behavior using Schottky
.include BC547.txt ;Including BJT model file
.include BAT54.txt ;Including Schottky model file
*Netlist
Q1 C B GND bc547a ;Defining the BJT Model Collector, Base, Emitter
X1 B C BAT54
Vin In 0 PULSE(0 5 0 0 0 5u 10u)
Rb In B 1k
Rc 2 C 1k
V_dd 2 0 5
*Transient Analysis
.tran 0.01u 0.04m
.control

```

```

run
set color0 = white
set color1 = black
set color2 = blue
set xbrushwidth = 2
plot V(C) V(In)
.endc
.end

```

## 3.2 Simulation results


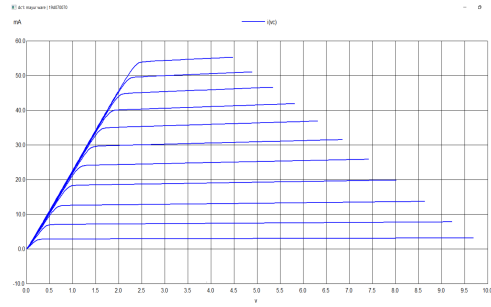


Fig. 4 :  $I_C$ - $V_{CE}$  of BJT in CE configuration

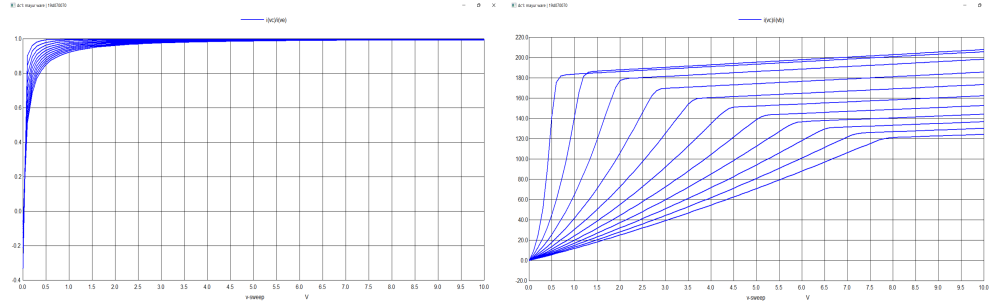

BJT in CE configuration

Fig. 5 :  $\alpha$ - $V_{CE}$

Fig. 6 :  $\beta$ - $V_{CE}$

Fig. 4, Fig. 5 and Fig. 6 show the overall characteristics of BJT in CE configuration.  $\alpha$  approaches to 1 with increase in  $V_{CE}$ . Whereas,  $\beta$  first linearly increases upto a point and then gets almost constant. Slopes of these curves determine threshold voltage ( $V_A$ ).

$\alpha = 0.9952$ ,  $\beta = 208.45$ ,  $R_B = 0.4992$  and  $V_A = -71.15V$ .




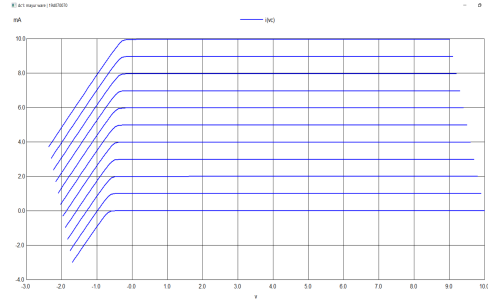


Fig. 7 :  $I_C$ - $V_{CB}$  of BJT in CB configuration

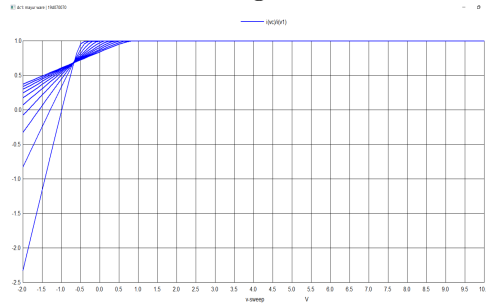

BJT in CB configuration

Fig. 8 :  $\alpha$ - $V_{CB}$

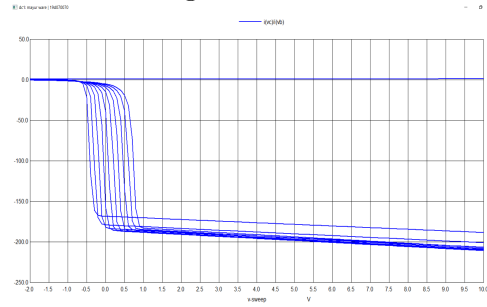


Fig. 9 :  $\beta$ - $V_{CB}$

Fig. 7, Fig. 8 and Fig. 9 show the overall characteristics of BJT in CB configuration.  $\alpha$  approaches to 1 with increase in  $V_{CB}$ . Whereas,  $\beta$  first decreases upto a point and then gets almost constant.

$\alpha = 0.9949$ ,  $\beta = 197.82$ ,  $RB = 1.031$ .

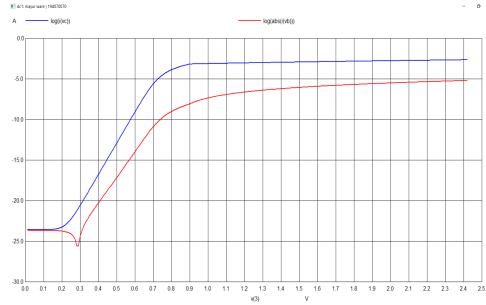


Fig. 10 : Gummel Plot

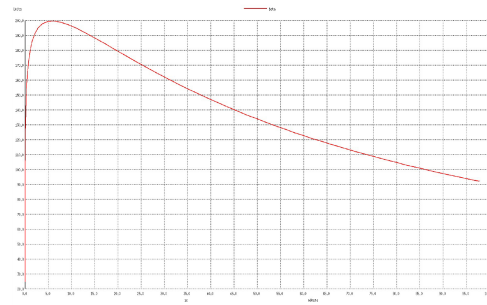


Fig. 11 :  $\beta_{DC}$ - $I_C$

Fig. 10 and Fig. 11 show the gummel plot and beta- $I_C$  plots respectively.

### Small Signal Paramters of BJT:

$$v(c) = 5.004189e+00$$

$$i(v_{cc}) = -4.49581e-03$$

$$i(v_{cc})/i(v_{bb}) = 1.974125e+02 \text{ Beta}$$

$$gm = -1.72916e-01$$

$$(i(v_{cc})/i(v_{bb}))/gm = -1.14167e+03 \text{ } r_{pi}$$

$$r_o = V_A/I_c = 15829.58843$$

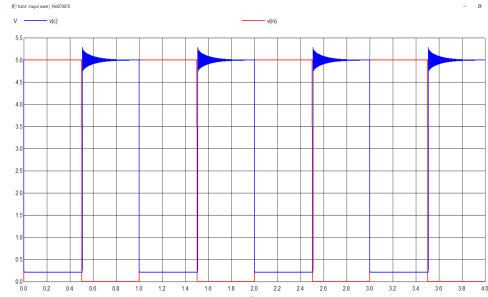


Fig. 12 : BC547 at f=1kHz

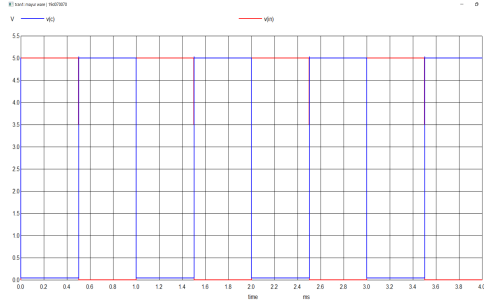


Fig. 13 : BC547 at f=100kHz

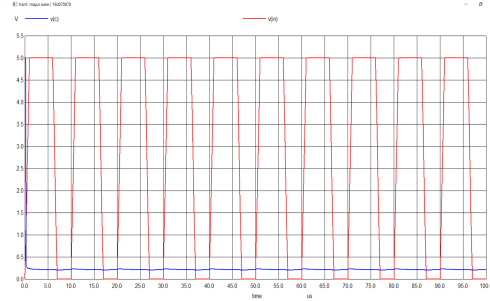


Fig. 14 : BC547 at f=1MHz

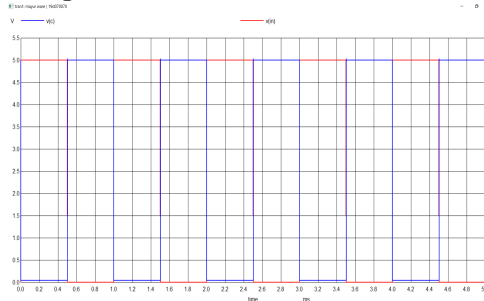


Fig. 15 : 2N3904 at f=100 kHz

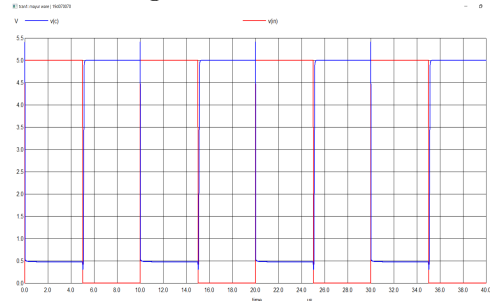


Fig. 16 : BC547 at f=1kHz with schottky diode

Fig. 12, Fig. 13, Fig. 14, Fig. 15 and Fig. 16 depict the switching behaviour

of two different types of BJTs BC547 and 2N3904 at different frequencies. Also, BC547 with schottky diode configuration. Table below tabulates the data of turnoff times.

Turnoff times in  $\mu$  sec.

Frequency	BC547	2N3904	BC547 with Schottky
1kHz	5.24	-	-
100kHz	4.68	0.36	0.09
1MHz	-	-	-

We can conclude that 2N3904 is faster than BC547. Also, schottky diode configuration is faster than the normal configuration.

## 4 Experimental results

This section is not applicable for this experiment.

## 5 Experiment completion status

I have completed all sections as well as exercises in this lab.

## 6 Questions for reflection

This section is not applicable for this experiment.

■