



Indian Institute of Technology, Bombay
Department of Electrical Engineering
Electronic Devices Lab(EE-236)

Quiz 1, Date: Feb 02, 2022

Timing: 2:00 PM to 4:00 PM

Spring 2022

Max marks: 10

1 Instructions

- You are allowed to use only those models that have been provided. You can download by clicking the name.
- You need not edit any model file.
- You can use previous lab report, netlist.

2 Problem Statements

1. You have been given a full wave precision rectifier circuit (see Figure 1) and a subcircuit model, let's call it black_box. Your task is as follows,

- Understand the given model (i.e. black_box). Use it to write the netlist of the given circuit (see Figure 1). **(1.5 Marks)**
- Plot the output response (V_{out}) of the circuit for sine input of **1 Vpeak** and frequency **1 kHz**. **(0.5 Marks)**
- Plot the transfer characteristics (V_{out} vs V_{in}) of this circuit and comment how transfer characteristics different from that of a full wave rectifier made using **1N4007 (Si diode)**. **(0.5 + 0.5 Marks)**

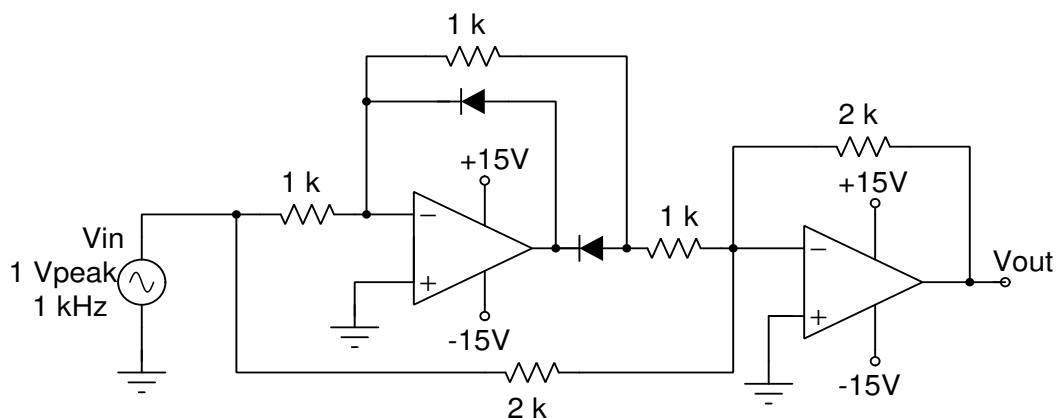


Figure 1: Circuit Diagram

The following models are given to you (Click on the names)

- OpAmp-UA741.
- Black Box

2.
 - In this particular part, we want you to plot I-V characteristics of two different diodes. These are fabricated from different materials, let's call them **X** and **Y**. **(0.5 Marks)**
 - You are expected to tabulate **Forward Voltage, Reverse Saturation Current, Peak Inverse Voltage(PIV) and Ideality factor** of each diode. Note your observations and comment. **(2 Marks)**
 - Bandgap of Silicon is **1.14eV** and bandgap of Germanium is **0.67eV**.
 - Suggest an application where one can use diode **X**, instead of diode **Y**. **(0.5 Marks)**

The following models are given to you (Click on the names)

- Diode X.
- Diode Y.

3.
 - Plot and comment on C_{DUT} vs $|V_{DUT}|$ characteristics of a **Schottky diode**, where C_{DUT} is junction capacitance and $|V_{DUT}|$ is reverse voltage. **(2 Marks)**
 - Similarly, plot $1/C^2$ vs V_{DUT} of a Schottky diode. Find doping density (N_D in $atoms/cm^3$) and diode's built in potential (V_{bi} in volts) from the plot. **You may refer equations mentioned in page 3. (2 Marks)**

NOTE:

- Here C is normalized junction capacitance= $C_{DUT}/Area$
consider Area= $1\mu m \times 1\mu m$ (Hypothetical value)

Purpose of small sinusoidal input signal:

- The capacitance at any given DC reverse bias is obtained by varying the charge around that corresponding depletion region edge by adding a small sinusoidal ac signal (1 Vpp, 100 kHz).
- Here TL071 is a high-speed JFET based operational amplifier (use $\pm 15V$ supply voltage) and design under test (DUT) is a Schottky diode.

The following models are given to you (Click on the names)

- Schottky diode: BAT85
- Op-Amp: TL071

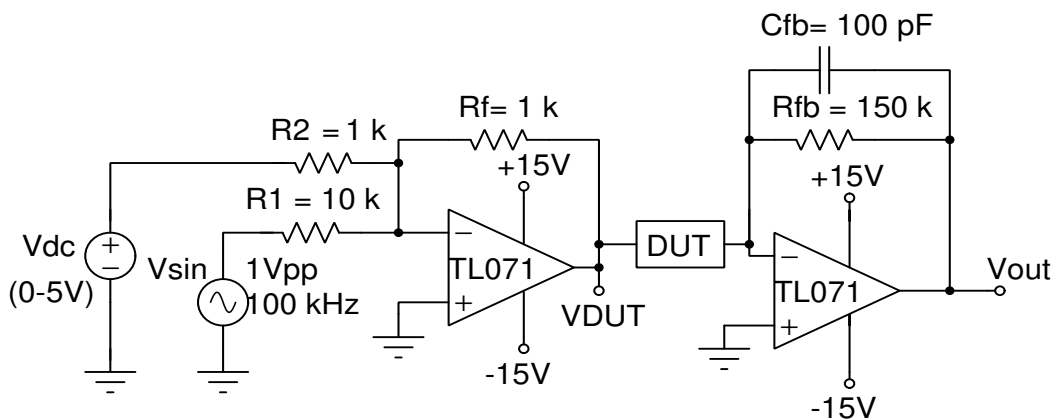


Figure 2: Circuit for measurement of C-V characteristics of a Schottky diode.

Formulas

- Transfer function : $|V_{out}/V_{DUT}| = (C_{DUT}/C_{fb})(1/\sqrt{1 + 1/(\omega \cdot R_{fb} \cdot C_{fb})^2})$
- $1/C^2 = (2/q\varepsilon N_D)(V_{bi} - V_R)$ where V_{bi} is diode built in potential
- V_R is diode reverse voltage = V_{DUT}
- $\varepsilon = \epsilon_0 \cdot \epsilon_{silicon} = 8.85 * 10^{-12} F/m * 11.7 = 1.03 * 10^{-10} F/m$
- q is charge of electron = $1.602 * 10^{-19}$ coulombs
- N_D is doping density, C is diode junction capacitance per unit area = $C_{DUT}/Area$