

Study of NMOS and CMOS Characteristics

Wadhwani Electronics Lab

EE 236: Electronic Devices Lab
Department of Electrical Engineering
Indian Institute of Technology Bombay

The Problem Statement

In this experiment, we will do the following:

- * Measure NMOS output and transfer characteristics
- * Investigate the effect of body bias on the characteristics of a NMOS transistor
- * Measure voltage transfer characteristics of CMOS inverter
- * Measure transient characteristics of CMOS inverter

Part 1- I_D - V_{DS} Characteristics

1. Write ngspice netlist to plot the I_D - V_{DS} characteristics of NMOS with the voltage V_{GS} varied from 2.5 V to 4 V in steps of 0.5 V. You may vary V_{DS} from 0 V to 5 V (show all 4 curves on a single plot)
2. From these characteristics, obtain r_{DS} (linear region) for each value of V_{GS} . Also, find "Early voltage" and r_0 in saturation region (considering channel length modulation)

Part 2- I_D - V_{GS} Characteristics in different regions

1. Estimate the value of threshold voltage and transconductance g_m in **linear region**:
 - Bias the transistor in linear region by keeping $V_{DS} = 200$ mV
 - Now write ngspice netlist to plot I_D v/s V_{GS} characteristics by varying V_{GS} from 0 to 5 V
 - From this characteristic, obtain V_T and g_m
2. Estimate the value of threshold voltage in **saturation region**:
 - Bias the transistor in saturation region by keeping $V_{DS} = 5$ V
 - Now write ngspice netlist to plot I_D v/s V_{GS} characteristics by varying V_{GS} from 0 to 5 V
 - From this characteristic, obtain V_T
 - Also, plot $\sqrt{I_D}$ v/s V_{GS} to find parameter K(mention its unit)

Part 3- Effect of Body Bias


1. Bias the transistor in linear region by keeping $V_{DS} = 200$ mV
2. Now write ngspice netlist to plot I_D v/s V_{GS} characteristics by varying V_{GS} from 0 to 5 V for $V_{SB} = 0$ V. (which is already asked in part 2)
3. Repeat the above step to get four more sets of I_D v/s V_{GS} characteristics for $V_{SB} = 1, 2, 3,$ and 4 V
4. Show all five I_D v/s V_{GS} characteristics on the same plot.
5. Obtain the value of threshold voltage from each plot
6. Plot V_T v/s V_{SB} and Obtain body effect coefficient (γ) using below equation. comment on dependence of V_T on V_{SB}

$$V_T = V_{T0} + \gamma(\sqrt{\phi_s + V_{SB}} - \sqrt{\phi_s})$$

where ϕ_s is Surface Potential = 0.9 V for ALD1105N NMOS model,
Threshold voltage (V_T) = V_{T0} when $V_{SB} = 0$ V

CMOS Inverter

 1. Write ngspice netlist for static CMOS inverter with load capacitance 0.05pF and VDD= 3.3 V. Logic low is 0V, logic High is 3.3V
2. specify source and drain capacitance using below information:
 source/drain area = $2 * W * L_{min}$
 source/drain perimeter = $2(W + 2 * L_{min})$



3. use the below template for instantiating nmos:
 mn drain gate source body cmosn $L=0.4\mu$ $W=W_n$ $AS=2*W_n*L$
 $PS=2*W_n+4*L$ $AD=2*W_n*L$ $PD=2*W_n+4*L$
4. Plot Voltage Transfer Characteristics(VTC) i.e V_{out} vs V_{in} for
 $W_p/W_n = 60\mu m/30\mu m$, $L = 0.4\mu m (= L_{min})$
5. Find out switching threshold from VTC curve

CMOS Inverter: Voltage Transfer Characteristics

1. Now take $W_p/W_n = 60\mu m/60\mu m$ and $W_p/W_n = 30\mu m/60\mu m$ and plot voltage transfer characteristics on a single plot along with the plot for $W_p/W_n = 60\mu m/30\mu m$. Comment on VTC curves behaviour and switching threshold.
2. Change the supply voltage V_{DD} to 1.5V, 3V for $W_p/W_n = 60\mu m/30\mu m$ and obtain all VTC curves on a single plot. Comment on the plots

CMOS Inverter: Transient Characteristics

1. Input square wave signal of frequency 125MHz with rise time and fall time of 20ps to CMOS inverter having load capacitance($C_L=0.05\text{pF}$) and $V_{DD}=3.3\text{V}$
2. **Rise delay(t_r):** t_r is time to rise output from 10% value to 90% value
Fall delay(t_f): t_f is time to fall output from 90%value to 10% value
Propagation delay (t_p): Measures speed of output reaction to input change

$$t_p = (t_{pf} + t_{pr})/2$$

- Fall propagation delay, t_{pf} is time for output to fall by 50% with reference to input change by 50%
 - Rise propagation delay, t_{pr} is time for output to rise by 50% with reference to input change by 50%
3. Find rise, fall, propagation delays for
 $W_p/W_n = 60\mu\text{m}/30\mu\text{m}$, $W_p/W_n = 60\mu\text{m}/60\mu\text{m}$, $W_p/W_n = 30\mu\text{m}/60\mu\text{m}$ and comment on each obtained values
 4. Vary the supply voltage from 2V to 3.3V and plot propagation delay vs. supply voltage(V_{DD}) for $W_p/W_n = 60\mu\text{m}/30\mu\text{m}$ and comment on the plot
Note: While changing supply voltage change input square wave voltage respectively