

Lab 4: Temperature dependance of Solar cell characteristics

Wadhwani Electronics Lab

Department of Electrical Engineering
Indian Institute of Technology, Bombay.

Part 1: I-V characteristics of Solar cell

- Modify the netlist written for I/V characteristics of a solar cell in the previous lab.
- Run the simulation to measure the dark forward characteristics at 35°C , 45°C , 55°C , 65°C , and 75°C .
- Note the values of V_D for $I_D=1\text{mA}$, 2mA and 5mA .
- Fill up in the observation table 1 below. Calculate η for low forward bias (1mA) and for high forward bias (5mA) at all the temperatures.

Sr.No	V_D for $I_D=1\text{mA}$	V_D for $I_D=2\text{mA}$	V_D for $I_D=5\text{mA}$	η for $I_D=1\text{mA}$	η for $I_D=5\text{mA}$
35°C					
45°C					
55°C					
65°C					
75°C					

Table 1

Note:-Refer ngspice commands to run simulation at different temperature.

Part-2: Lighted I/V Characteristics

In this part, we will plot the I/V characteristics of the solar cell when used as a power source. We will measure I/V characteristics at various temperatures when the solar cell is lighted at the intensity to generate $I_L=8\text{mA}$.

- A load resistor R is connected across the solar cell same as you have done in the previous lab. The value of R is varied from 1 to 500Ω and the values of I_R and V_R are recorded for the temperatures 35°C to 75°C in steps of 10°C .
- Plot I_D - V_D and P_R - V_D characteristics under lighted condition at all the temperatures. Note the values of V_{oc} and I_{sc} values for all temperatures.
- Obtain Fill Factor (FF) for all the temperature and plot FF v/s temperature.
- Plot V_D v/s Temp and V_{oc} v/s Temp. You will get three sets of V_D for $I_D = 1\text{mA}$, 2mA and 5mA obtained in Part-1.
- Comment on the dependence of V_{oc} , I_{sc} , and FF.

Part-3:Effect of R_S and R_{sh}

- Plot I/V characteristics for series resistance $R_S = 0, 10, \text{ and } 30 \, \Omega$. You may plot the part of characteristic in fourth quadrant, in the first quadrant for convenience if you should.
- How the I/V characteristics of solar cell is affected by the series resistance R_S ?
- Plot I/V characteristics for shunt resistance $R_{sh} = 100 \, \Omega, 500 \, \Omega, \text{ and } 5 \, \text{K}\Omega$.
- What do you observe? What is effect of larger values of shunt resistance on the performance of the solar cell?
- Also plot V_{oc} , I_{sc} and fillfactor versus R_S and R_{sh} and comment on dependence of these parameters on R_S and R_{sh}

Note:- R_S and R_{sh} are the series and shunt resistances of the solar cell hence their values should be varied in the model file to observe the effect.